

Ex: 7



United International University

School of Science and Engineering

Quiz 1 Year 2021 Semester: Summer
Course: PHY 106 / PHY 2106 Title: Physics Lab
Full Marks: 7.5 Section: A Time: 20 Min

- Q01. Determine the current using Ammeter by increasing supply voltage by an amount 5V, 10V, 15V, 20V, 25V with a total resistance of $100\ \Omega$ _____ in Ohm's law Experiment.
- Q02. Determine the current using Ammeter by constant supply voltage 40V for a total resistance of $20\ \Omega$ and 30, 40, 50, 60, $80\ \Omega$ in Ohm's law Experiment.
- Q03. Determine the resistance from I-V graph of current-voltage data and also compare your result when Known R_T is $80\text{K}\Omega$.
- Q04. Determine the resistance from I-V graph of current-voltage data and also compare your result when Known R_T is $110\text{K}\Omega$.
- Q05. Determine the voltage and Verify Ohm's law from I- R_T graph and also compare your result with supply voltage 25V.
- Q06. Determine the value of "g" using "L=60cm" and time period of oscillation of _
3_____ no hole of the compound pendulum.
- Q07. Determine the value of "g" using "L=60cm" and time period of oscillation of _
5_____ no hole of the compound pendulum.