



United International University

School of Science and Engineering

Quiz 2 Year 2021 Semester: Summer
Course: PHY 2106 Title: Physics Lab
Full Marks: 7.5 Section: A Time: 15 Min

Q01. Determine the diameter of Newton's 5th ring.

Q02. Determine the diameter of Newton's 7th ring.

Q03. Determine the radius of curvature of the lens from the data found from 2nd and 8th rings from the graph.

Q04. Determine the radius of curvature of the lens from the data found from 3rd and 7th rings from the graph.

Q05. Find the voltage drops in three resistances of 120Ω , 90Ω , and 20Ω for $15V$ supply and verify KVL. Also compare your result with supply voltage.

Q06. Determine the total current and current passing in each resistor in a given circuit consisted with two resistances of 10Ω and 40Ω . Given the voltage supply is $70V$. Verify KCL. Given the Total current is $20mA$. Also compare your result with the given current.

Q07. Determine the measured voltage drop across resistor in KVL experiment for the resistances of 100Ω , 220Ω , and 470Ω and supply voltage $20V$. Compare your result.

Q08. Determine the measured current across resistor in KCL experiment for the resistances of 60.5Ω , 80.5Ω , and 90.5Ω and Supply voltage $37V$.

