

Nominal Values of Resistance (R)	Measurement Values of Resistance by (r)	$R = R_1 + R_2 + R_3$	Measured Voltage across each resistor	Calculate Voltage
100 Ω				
220 Ω	790	790	$V_1 = 2.53$	$V_1 = 2.53$
470 Ω	790	790	$V_2 = 5.57$	$V_2 = 5.57$
	790	790	$V_3 = 11.9$	$V_3 = 11.9$
			$V = 20$	$V = 20$

Name: Md. Mehedi Hassan

ID: 011201205

Sec: A

$$V_1 = \frac{R_1}{R_T} \times 20 = 2.53$$

$$V_2 = \frac{R_2}{R_T} \times 20 = 5.57$$

$$V_3 = \frac{R_3}{R_T} \times 20 = 11.9$$

$$V_{\text{supply}} = V_1 + V_2 + V_3 \quad \text{Verified}$$

