

Name: Md. Mehedi Hassan

ID: 011201205

L No: Ans:

<u>Supply (V)</u>	<u>Measured by using Ammeter (A)</u>	<u>Resistor 100</u>	<u>Calculate (A)</u> $I = \frac{V}{R}$
5 →	0.5 →	100 →	0.5
10 →	0.1 →	100 →	0.1
15 →	0.15 →	100 →	0.15
20 →	0.2 →	100 →	0.2
25 →	0.25 →	100 →	0.25

So, The table indicates that, if V increased and Resistor is fixed, then current (I) will be increased.